
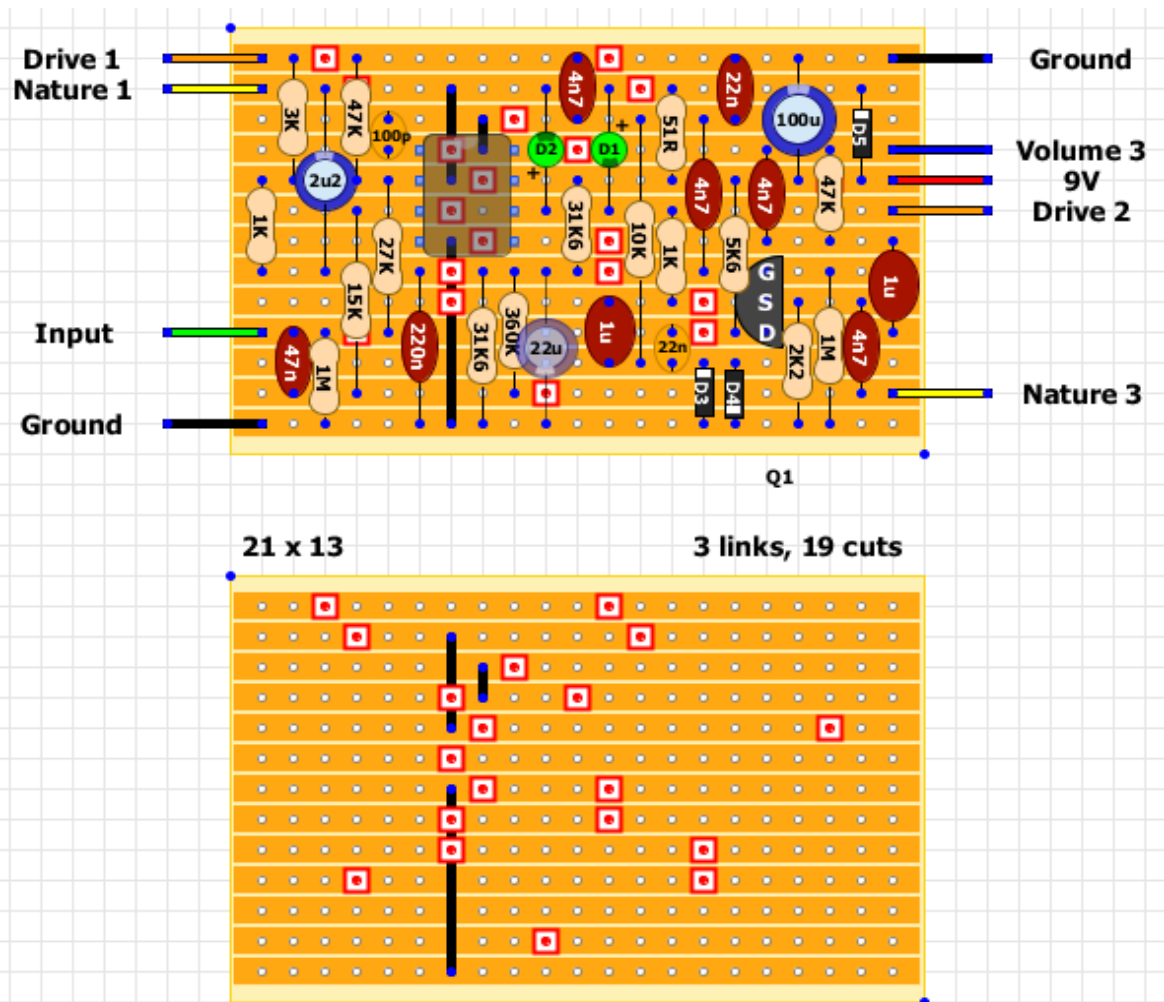


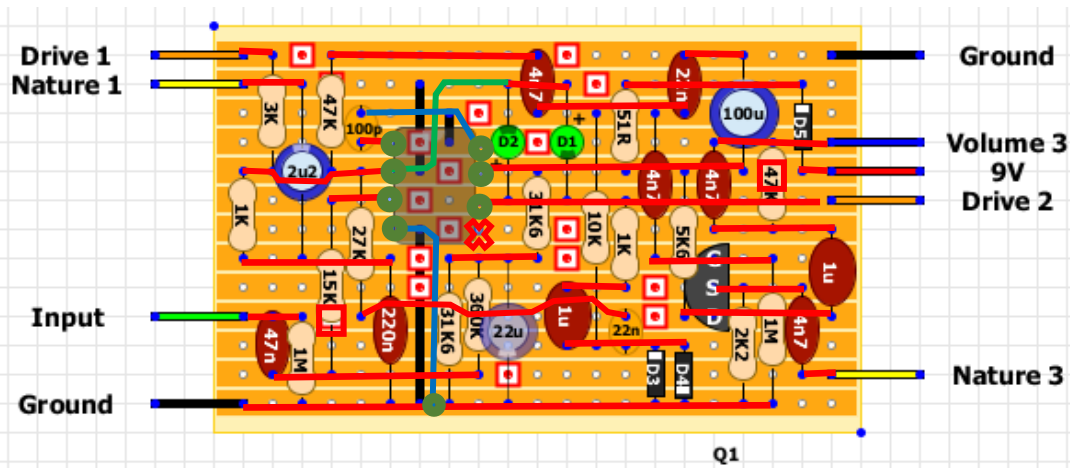

IC is CA3130  
 Q1 is 2N5457  
 D1 & D2 are green LEDs  
 D3 & D4 are 1N4007 (use 1N4001)  
 Drive 500kA, Nature 50kA, Volume 50kA  
 Nature 2 and Volume 1 to ground, Volume 2 to output


**BJFE Honeybee - Layout 2**  
 IvIark © <http://taqboardeffects.blo>





21 x 13

3 links, 19 cuts

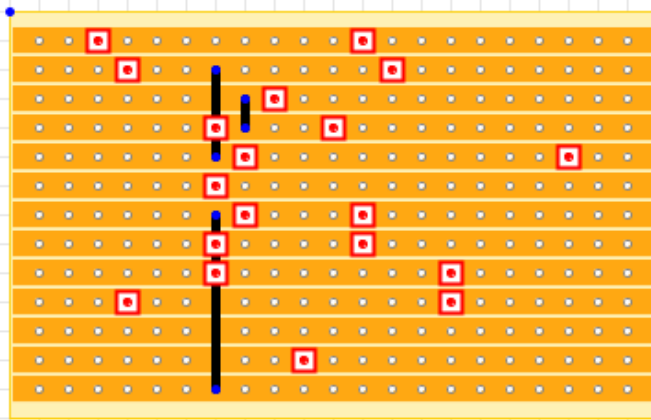

IC is CA3130

Q1 is 2N5457

D1 & D2 are green LEDs


D3 & D4 are 1N4007 (use 1N4001)


Drive 500kA, Nature 50kA, Volume 50kA

Nature 2 and Volume 1 to ground, Volume 2 to output

**BJFE Honeybee - Layout 2**

IvIark © <http://taqboardeffects.blo>

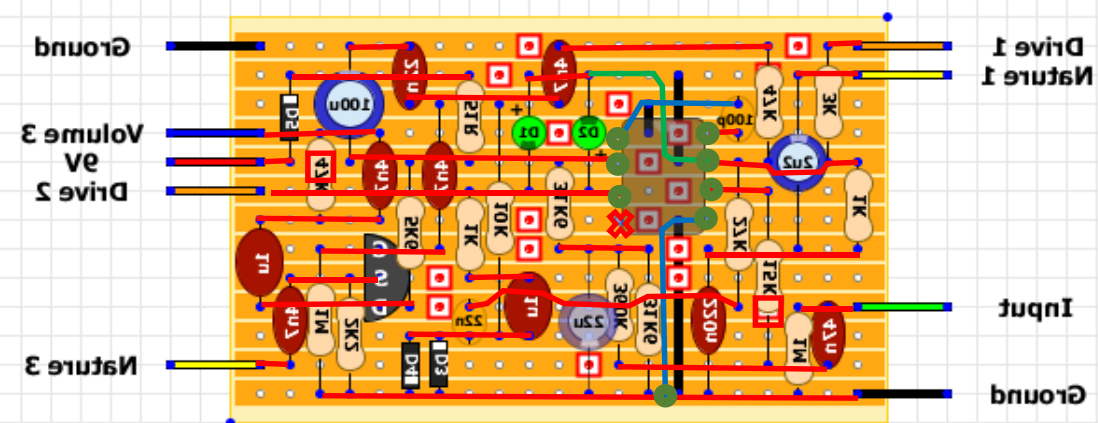

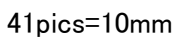

*Actual size(実寸大)*